# National Cheng Kung University Department of Electrical Engineering

## Introduction to VLSI CAD (Spring 2024)

## **Lab Session 2**

# Design and Simulation of Carry-Lookahead Adder & Parallel-Prefix Adder & Multiplier

Name		Student	ID
鄭喆嚴	E14096724		
Practical Sections:		Points	Marks
Prob A		15	
Prob B		30	
Prob C		40	
Report		15	
Bonus		10	
Notes			

#### Due Date: 14:59, March 13, 2024 @ moodle

#### **Deliverables**

- All Verilog codes including testbenches for each problem should be uploaded.
   NOTE: Please **DO NOT** include source code in the paper report!
- 2) All homework requirements should be uploaded in this file hierarchy or you will not get the full credit.
  - NOTE: Please DO NOT upload waveforms!
- 3) Important! TA will use the command in Appendix A to check your design under SoC Lab environment, if your code can not be recompiled by TA successfully using the commands, you will not get the full credit.
- 4) If you upload a dead body which we can't even compile you will get NO credit!
- 5) All Verilog file should get at least 90% superLint Coverage.
- 6) File hierarchy should not be changed; it may cause your code can not be recompiled by TA successfully using the autograding commands

 


Fig.1 File hierarchy for Homework submission


#### **Objectives:**

Help students get familiar with the CAD tools (VCS & Verdi) for digital logic design. Introduce different adder architectures and the algorithms behind them. Please go through the hands-on exercise step-by-step.


- 1) An adder is a digital circuit that performs addition of number. Please design a full adder in gate level.
- 2) The truth table of full adder

Inputs			Outputs		
Α	В	c <sub>in</sub>	cout	s	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	
1	0	0	0	1	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	

3) Draw a full adder in gate level.

 

 
- 4) Design a full adder in Structural coding (The module name should be FA. And the file you include should be FA.v)
- 5) Carry-lookahead-adder uses carry generator to alleviate the lengthy carry propagation procedure in ripple-carry-adder.
- 6) Derive the  $8^{th}$  carry bit  $C_8(ex. C_2 = A_1B_1 + (A_1 + B_1)C_1 = g_1 + p_1C_1 = g_1 + p_1g_0 + p_1p_0C_0)$



ex.  $C_2 = A_1B_1 + (A_1 + B_1)C_1 = g_1 + p_1C_1 = g_1 + p_1g_0 + p_1p_0C_0$ ,  $g_1 + p_1g_0 + p_1p_0C_0$  is the final result

 $C_8 = A_7B_7 + (A_7 + B_7)C_7 = g_7 + p_7C_7 = g_7 + p_7g_6 + p_7p_6C_6 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5C_5$ 

- $= g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4C_4$
- $= g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3C_3$
- $= g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2C_2$
- $= g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1C_1$
- $= g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0C_0$
- 7) **Design a 8-bit carry lookahead adder** in **Structural coding** (The module name should be CLA8. And the file you include should be CLA8.v)
- 8) **Design a 32-bit carry lookahead adder in hierarchical coding** using previously designed CLA8 module. (The module name should be CLA32. And the file should be CLA32.v)

 

Page 5 of 18


Signal	10	Bits	Description
а	Input	32	Addend
b	Input	32	Augend
sum	Output	32	Result after calculating
overflow	Output	1	Overflow detection

- 9) Simulate your design with the following test pattern in sample testbench. (Hint: The command for compiling is % vcs -R tb\_CLA.32v -full64) (Hint: The command for simulation is %vcs -R tb\_CLA32.v -debug\_access+all -full64 +define+FSDB)
- 10) Verify your design by comparing the simulation results with the results you predicted. If the results are not the same, please go back to 2) and revise your code. If the simulation results are correct, please snapshot the simulation result on the terminal and the waveform you dumped and explain your waveform.

  (Hint: The command to open nWave is %nWave &)

  In addition, you should check your coding style, and make sure that there are no error messages and coverage with Superlint must > 90 %. Snapshot the result and calculate Superlint coverage. (Hint: The command to open Superlint is %jg -superlint superlint.tcl)
- 11) You only need to upload your v-code to moodle, do not paste your code here.
 
#### Your simulation result on the terminal.




#### Your waveform:


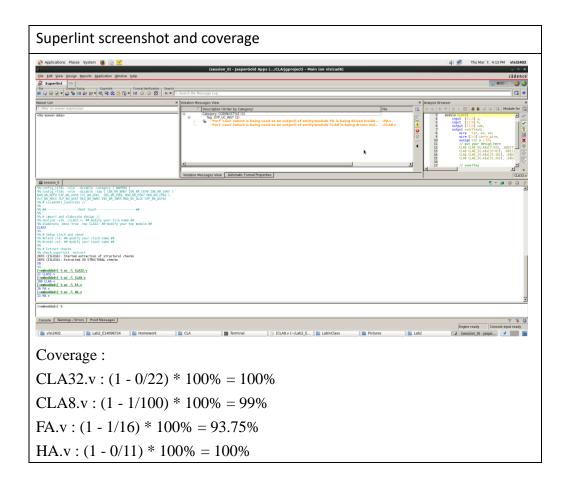
#### Explanation of your waveform:

上面波形圖 error 一直都為 0,代表全部的測資皆正確。

下面波形圖中可以看到所有測資皆有執行加法,並且加法的結果和 overflow 皆與測資的答案相同。



- 1) Parallel-prefix-adder reduces the complexity of the carry generation circuitry in carry-lookahead-adder.
- 2) Recursive formulation of carry bits:

Q(m, n) = 
$$\sum_{i=n}^{m} (\prod_{r=i+1}^{m} p_r) g_i$$

$$C_{0} = 0$$

$$C_{1} = A_{1}B_{1} + (A_{1} \oplus B_{1})C_{0} = g_{1} + p_{1}C_{0} = g_{1}$$

$$C_{2} = A_{2}B_{2} + (A_{2} \oplus B_{2})C_{1} = g_{2} + p_{2}C_{1} = g_{2} + p_{2}g_{1}$$

$$C_{3} = A_{3}B_{3} + (A_{3} \oplus B_{3})C_{2} = g_{3} + p_{3}C_{2} = g_{3} + p_{3}g_{2} + p_{3}p_{2}g_{1}$$


$$= Q(2, 1) = p_{2}Q(1, 1) + Q(2, 2)$$

$$= Q(3, 1) = p_{3}p_{2}Q(1, 1) + Q(3, 2)$$

$$= p_{3}p_{2}Q(1, 1) + p_{3}Q(2, 2) + Q(3, 3)$$


$$C_{4} = A_{4}B_{4} + (A_{4} \oplus B_{4})C_{3} = g_{4} + p_{4}C_{3} = g_{4} + p_{4}g_{3} + p_{4}p_{3}g_{2} + p_{4}p_{3}p_{2}g_{1}$$
 
$$= Q(4, 1) = p_{4}p_{3}Q(2, 1) + Q(4, 3)$$



 - 3) Design a full adder in Structural coding (The module name should be FA. And the file you include should be FA.v)
- 4) **Design black cell & blue cell in Structural coding** (The module name should be black\_cell & blue\_cell. And the file you include should be black\_cell.v & blue cell.v)
- 5) Design a 8-bit parallel-prefix-adder in hierarchical coding using black cell & blue cell as basic unit (The module name should be PPA8. And the file you include should be PPA8.v)
- 6) **Design a 32-bit parallel-prefix-adder in hierarchical coding** using previously designed PPA8 module. (The module name should be PPA32. And the file should






Signal	10	Bits	Description
а	Input	32	Addend
b	Input	32	Augend
sum	Output	32	Result after calculating
overflow	Output	1	Overflow detection

- 7) Simulate your design with the following test pattern in sample testbench. (Hint: The command for compiling is % vcs -R tb\_PPA32.v -full64) (Hint: The command for simulation is %vcs -R tb\_PPA32.v -debug\_access+all -full64 +define+FSDB)
- 8) Verify your design by comparing the simulation results with the results you predicted. If the results are not the same, please go back to 2) and revise your code. If the simulation results are correct, please snapshot the simulation result on the terminal and the waveform you dumped and explain your waveform. (Hint: The command to open nWave is %nWave &)
  In addition, you should check your coding style, and make sure that there are no error messages and coverage with Superlint must > 90 %. Snapshot the result and calculate Superlint coverage. (Hint: The command to open Superlint is %jg -superlint superlint.tcl)
- 9) You only need to upload your v-code to moodle, **do not** paste your code here.
 
#### Your simulation result on the terminal.




#### Your waveform:


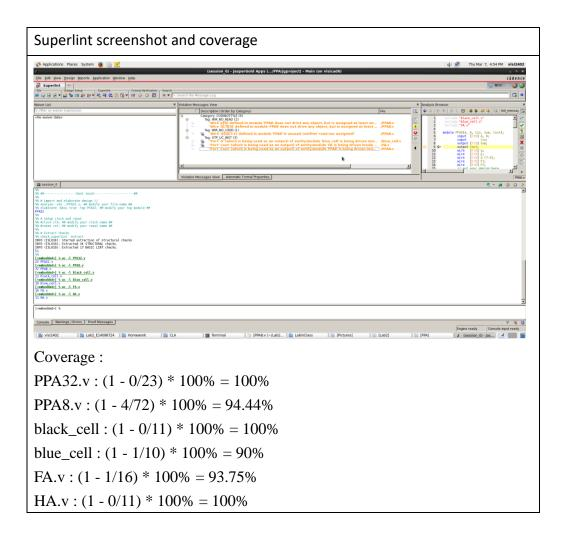
#### Explanation of your waveform:

上面波形圖 error 一直都為 0,代表全部的測資皆正確。

下面波形圖中可以看到所有測資皆有執行加法,並且加法的結果和 overflow 皆與測資的答案相同。




#### Prob C: Application


- 1) Design a 8\*8-bit multiplier
  - a. Using CLAs of Prob A
  - b. Using PPAs of Prob B
  - c. Design in gate level rather than behavioural modelling. (The module name should be Multiplier\_CLA & Multiplier\_PPA. And the file you include should be Multiplier CLA.v & Multiplier PPA.v)
- 2) Draw your hieratical structure.
- 3) You only need to upload your v-code to moodle, do not paste your code here.
- 4) Simulate your design with the testbench which includes all case of input. (Hint: The command for compiling is % vcs -R tb\_Multiplier.v -full64) (Hint: The command for simulation is % vcs -R tb\_Multiplier.v -debug access+all -full64 +define+FSDB)
- 10) Verify your design by comparing the simulation results with the results you predicted. If the results are not the same, please go back to 2) and revise your code. If the simulation results are correct, please snapshot the simulation result on the terminal and the waveform you dumped and explain your waveform. (Hint: The command to open nWave is %nWave &)

  In addition, you should check your coding style, there are no error messages and over 90% coverage with Superlint. Snapshot the result and calculate Superlint coverage. (Hint: The command to open Superlint is %jg -superlint superlint.tcl)

Using CLAs Design a 8\*8-bit multiplier

 

## Your waveform :

 


#### Explanation of your waveform:

上面波形圖 error 一直都為 0,代表全部的測資皆正確。

下面波形圖中可以看到所有測資皆有執行乘法,並且乘法的結果皆與測資的答案相同。

#### Superlint screenshot and coverage

 

#### Coverage:


Multiplier\_CLA.v : (1 - 0/113) \* 100% = 100%

CLA8.v : (1 - 0/100) \* 100% = 100%

FA.v: (1 - 1/16) \* 100% = 93.75%

HA.v : (1 - 0/11) \* 100% = 100%
 
#### Using PPAs Design a 8\*8-bit multiplier




# Your waveform: Application Flace System & Sec. Sec. System & Sec. Syste

#### Explanation of your waveform:

上面波形圖 error 一直都為 0,代表全部的測資皆正確。

下面波形圖中可以看到所有測資皆有執行乘法,並且乘法的結果皆與測資的答案相同。

#### Superlint screenshot and coverage

 

#### Coverage:

Multiplier\_PPA.v : (1 - 0/113) \* 100% = 100%

PPA8.v: (1 - 3/72) \* 100% = 95.83% black\_cell: (1 - 0/11) \* 100% = 100% blue\_cell: (1 - 1/10) \* 100% = 90% FA.v: (1 - 1/16) \* 100% = 93.75%

HA.v : (1 - 0/11) \* 100% = 100%

 $Appendix\,A: Commands\ we\ will\ use\ to\ check\ your\ homework$ 

Problem		Con	nmands
ProbA	Compile	%	vcs -R tb_CLA32.v -full64
	Simulate	%	vcs -R tb_CLA32.v -debug_access+all -full64 +define+FSDB
ProbB	Compile	%	vcs -R tb_PPA32.v -full64
	Simulate	%	vcs -R tb_PPA32.v -debug_access+all -full64 +define+FSDB
ProbC	Compile	%	vcs -R tb_Multiplier.v -full64
	Simulate	%	vcs -R tb_Multiplier.v -debug_access+all -full64 +define+FSDB