National Cheng Kung University Department of Electrical Engineering

Introduction to VLSI CAD (Spring 2024)

Lab Session 4

Register Files, Manhattan Distance and LFSR

Name Student ID		ID
鄭喆嚴	E14096724	
Practical Sections	Points	Marks
Prob A	30	
Prob B	30	
Prob C	20	
Report	15	
File hierarchy, namingetc.	5	
Notes:		

Due Date: 15:00, March 27, 2024 @ moodle

Deliverables

- 1) All Verilog codes including testbenches for each problem should be uploaded. NOTE: Please **DO NOT** include source code in the paper report!
- 2) All homework requirements should be uploaded in this file hierarchy or you will not get the full credit.
 - NOTE: Please DO NOT upload waveforms!
- 3) Important! TA will use the command in Appendix A to check your design under SoC Lab environment, if your code can not be recompiled by TA successfully using the commands, you will not get the full credit.
- 4) If you upload a dead body which we can't even compile you will get NO credit!
- 5) All Verilog file should get at least 90% superLint Coverage.
- 6) File hierarchy should not be changed; it may cause your code can not be recompiled by TA successfully using the autograding commands


 


Fig.1 File hierarchy for Homework submission

Prob A: SIPO Register File

 

- 1. Based on the SIPO register file structure in LabA, please design a 128 x 32 SIPO register file with 5 output ports.
- 2. Port list

Signal	Туре	Bits	Description
clk	input	1	clock
rst	input	1	reset
reg_enable	input	1	register file enable
reg_write	input	1	$0 \rightarrow \text{read } 1 \rightarrow \text{write}$
src_addr	input	7	source address
write_addr	input	7	write address
write_data	input	32	write data
src1	output	32	read data source1
src2	output	32	read data source2
src3	output	32	read data source3
src4	output	32	read data source4
src5	output	32	read data source5

3. Show the simulation result on the terminal.



4. Show waveforms to explain that your register work correctly when read and write.

Read:



可以從波形中看到,當 reg_enable 為 1 且 reg_write 為 0,在 clock 上升時讀取 src_addr(hexadecimal:69,decimal:105)地址中的資料以及後四筆共五筆資料(src1~src5),可以從 register file 中看到讀取正確。


Write:



```
R[ 0] = ffff0000
R[ 1] = ffff0001
R[ 2] = ffff0002
R[ 3] = ffff0003
R[ 4] = ffff0004
```

可以從波形圖中看到,當 reg_enable 為 1 且 reg_write 為 1,在 clock 上升時在 write_addr(hexadecimal:0~5,decimal:0~5)地址寫入 write_data 資料,可以從 register file 中看到讀取正確。


5. Show SuperLint coverage

 

Coverage:

Regfile_sipo.v : (1 - 0/81) * 100% = 100%

Prob B: Finding Smallest Distance

 

1. Please design a circuit that will find the smallest distance between the input feature and input colors, based on the structure given in the LAB4 slide.

2. Port listManhattan:

Signal	Туре	Bits	Description
clk	input	1	Clock pin.
rst	input	1	Reset pin.
clear	input	1	Set all registers to 0.
c_en	input	1	Write compared colors enable. When c_en is high, then c_in0~7 is available.
if_en	input	1	Write input pixel enable. When if_en is high, then if_in is available.
c_in0~7	input	24 each	Input color data.
if_in	input	24	Input input feature data.
d_0~7	output	10 each	Output distance data.


Min:

Signal	Туре	Bits	Description
d_0~7	input	10 each	Input data.
out_index	output	3	Output index.
out_distance	output	10	Output minimum distance.

3. Show the simulation result on the terminal.




 4. Show waveforms to explain that your design works correctly.



可以從波形圖中看到,當 reg_enable 為 1 且 reg_write 為 1,在 clock 上升時在 write_addr(hexadecimal:0~5,decimal:0~5)地址寫入 write_data 資料,可以從 register file 中看到讀取正確。

5. Show SuperLint coverage

 

Coverage:

Manhattan.v : (1 - 0/134) * 100% = 100%

Min.v: (1 - 0/78) * 100% = 100%

top.v : (1 - 0/47) * 100% = 100%

Prob C: LFSR

1. Please design an 8-bit-LFSR, with the given feedback function in the LAB4 slide.


2. Port list

Signal	Туре	Bits	Description
clk	input	1	Clock pin.
rst	input	1	Reset pin. Reset all of the flip flops to zeros.
seed_val	input	1	the flip flops take seed as the initial state. the flip flops works as linear feedback shift register.
seed	input	8	Initial state value of LFSR.
d	output	8	Output value of LFSR

3. Feedback function


$d[0] = (d[7] \wedge d[5]) \wedge (d[4] \wedge d[2])$

 4. Show waveforms to explain that your LFSR module works correctly.




可以從上方的波形圖中看到,在 clock 上升時 d[0]~d[6]會向後傳遞到 d[1]~d[7],並且可以從下方的波形圖中看到 d[0]確實有依照 d[0] = (d[7] ^ d[5]) ^ (d[4] ^ d[2]) 來產生。

 5. Show the simulation result on the terminal.



6. Show SuperLint coverage

 

Coverage:

LFSR.v: (1 - 0/30) * 100% = 100%

At last, please write the lesson you learned from Lab4

這次的 Lab 讓我學習到有關 SIPO register file、Manhattan、Min 和 8-bit-LFSR 在硬體上設計,SIPO register file 讓我更了解了有關記憶體的運作,Manhattan 和 Min 也讓我學到計算顏色和顏色之間的距離和取最小值的作法,LFSR 也讓我學到亂數是可以用這種傳遞的方式來產生,另外這次的 Lab 讓我學習到如何修改程式來讓 superlint 中的錯誤和警告減少,像是如何修改程式來解決 propagation race、multiple drive 的問題,來讓我程式的 coverage 達到100%。

Appendix A : Commands we will use to check your homework

Problem		Command
2.14	Compile	% vcs -R regfile_sipo.v -full64
Prob A	Simulate	% vcs -R regfile_sipo_tb.v -debug_access+all -full64 +define+FSDB
Compile		% vcs -R top.v -full64
Prob B	Simulate	% vcs -R top_tb.v -debug_access+all -full64 +define+FSDB
Compile % vo		% vcs -R LFSR.v -full64
PIODC	Simulate	% vcs -R LFSR_tb.v -debug_access+all -full64 +define+FSDB